

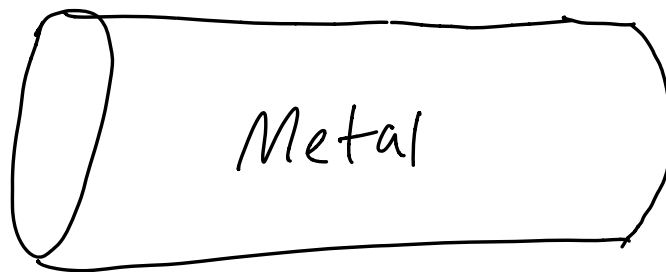

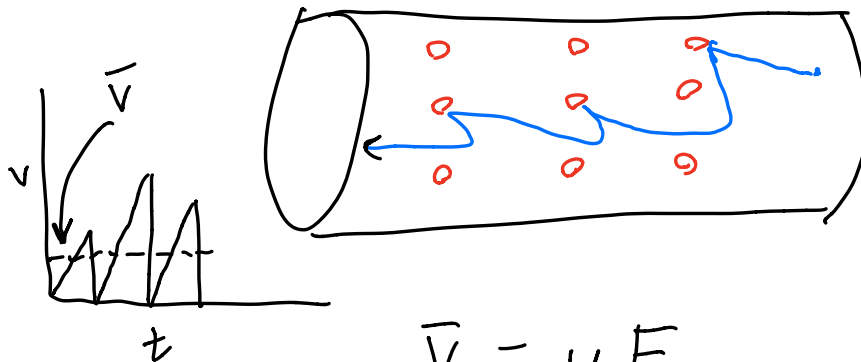
## Outline

- Review of charge motion in conductors
  - Electron velocity and electron current
- Equilibrium vs steady state
- Conservation of current: the node rule
- Thick and thin wires
  - Currents, velocities, fields



What happens?

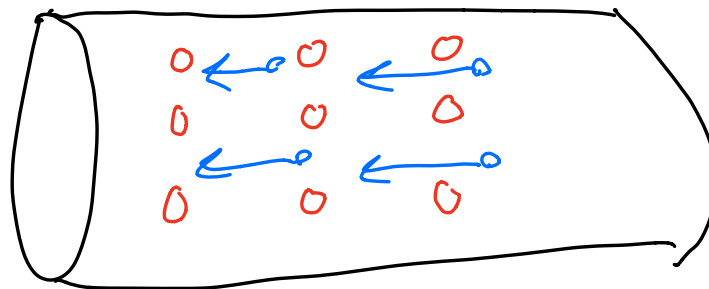

$$\bar{v} = uE$$

$$\bar{v} = u E$$


Drift Velocity  
e - Mobility

$$i = \#e/sec$$

$$i = n A \bar{v}$$

$$I = |q| i$$

A simple circuit

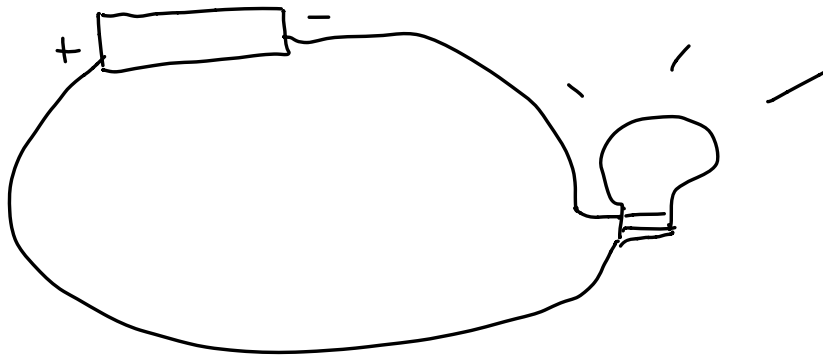

- What happens to the bulb?
- Are we in equilibrium?
- Not static  $E_g$ , but "Steady State"

## Charge Motion in Conductors

Static $E_q$	Steady State
$\bar{v} = 0$	$\bar{v} \neq 0$ (Not changing)
$i = 0$	$i \neq 0$
$E_{\text{net}} = 0$	$E_{\text{net}} \neq 0$
	} not changing

CQ

18.2.a

$-e^-$  move away from neg terminal

( Q 18.2.c

is the current used up in the bulb?

- Charge is conserved. Electrons cannot be destroyed.
- Charge does not pile up, current would eventually stop


current is same

NODE RULE:

$$i_{IN} = i_{OUT}$$

(conservation of charge + steady state)


A "node" is just a point on the circuit

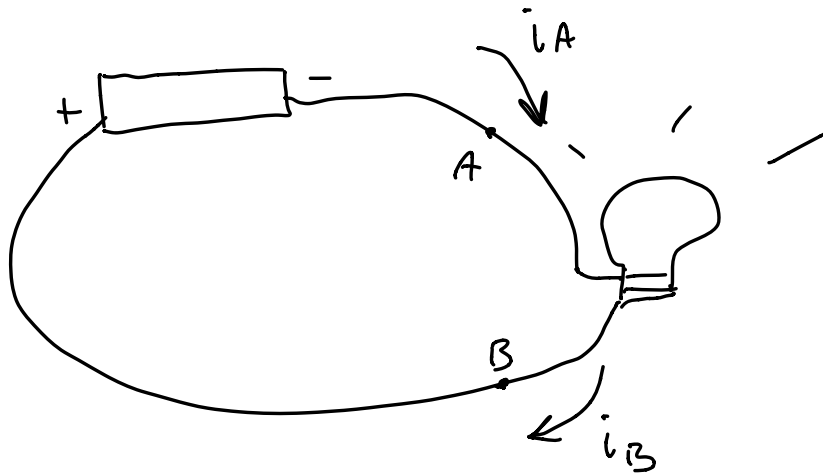

$$i_{IN} = i_A$$

$$i_{OUT} = i_B$$


$$i_A = i_B$$

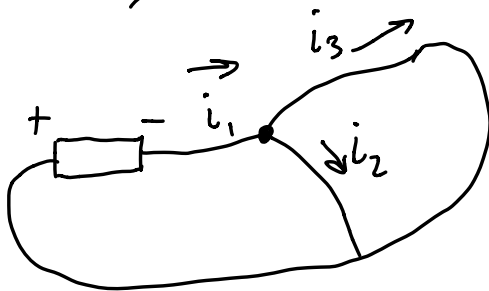

$$i_{IN} = i_1$$

$$i_{OUT} = i_2 + i_3$$

$$i_1 = i_2 + i_3$$

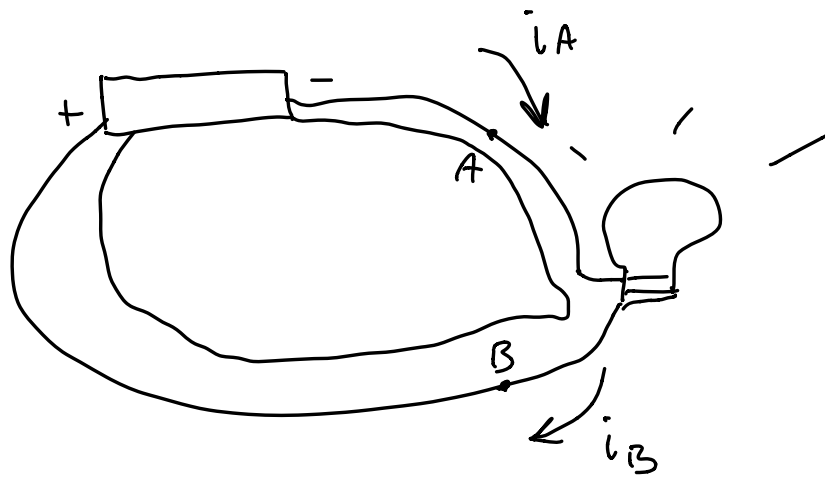


$$i_A = i_B \quad i = n A \bar{v}$$

$$n_A A_A \bar{v}_A = n_B A_B \bar{v}_B$$

$$\bar{v}_A = \bar{v}_B$$

CQ 18.2.d

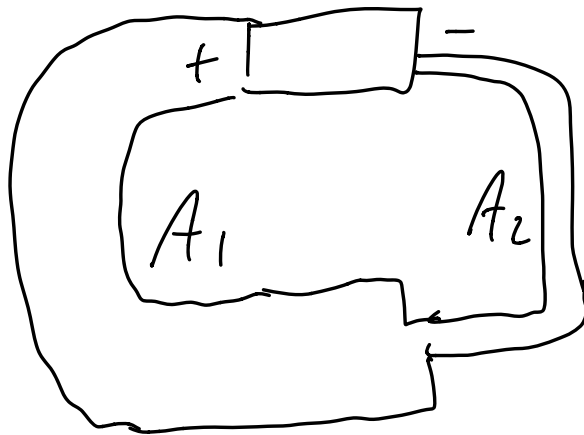

$$i_2 = i_1$$

$$v_1, v_2 ?$$

$$v_2 > v_1$$

$$n A_1 \bar{v}_1 = n A_2 \bar{v}_2$$

$$\bar{v}_1 = \frac{A_2}{A_1} \bar{v}_2, \quad \frac{A_2}{A_1} < 1$$

$$v_1 < v_2$$

(water in a pipe)



$$A_1 = 4 A_2$$

$$\bar{V}_1 = \frac{1}{4} \bar{V}_2$$

$$\vec{E}?$$

$$n_1 A_1 \bar{V}_1 = n_2 A_2 \bar{V}_2$$

$$\bar{V} = u E$$

$$n_1 A_1 u_1 E_1 = n_2 A_2 u_2 E_2$$

Same material

$$n_1 = n_2$$

$$u_1 = u_2$$

$$A_1 E_1 = A_2 E_2 \Rightarrow E_1 = \frac{A_2}{A_1} E_2$$

$$E_1 = \frac{1}{4} E_2$$

CQ 18.3e

$$i_1 = i_2$$

$$n_1 A_1 u_1 E_1 = n_2 A_2 u_2 E_2$$

$$A_1 = A_2$$

$$n_1 u_1 E_1 = n_2 u_2 E_2$$

$$E_1 = \frac{n_2 u_2}{n_1 u_1} E_2, \quad \frac{n_2}{n_1} = 3$$

$$E_1 = \frac{3u_2}{u_1} E_2$$