

LAB 6

MACROSCOPIC CIRCUIT ANALYSIS


OVERVIEW

Main point of today's lab:


- Build different types of resistor circuits
- Use the loop/node rule to predict the current and voltage of each resistor
- Measure the current and voltage of each resistor, and compare results

BREADBOARDS


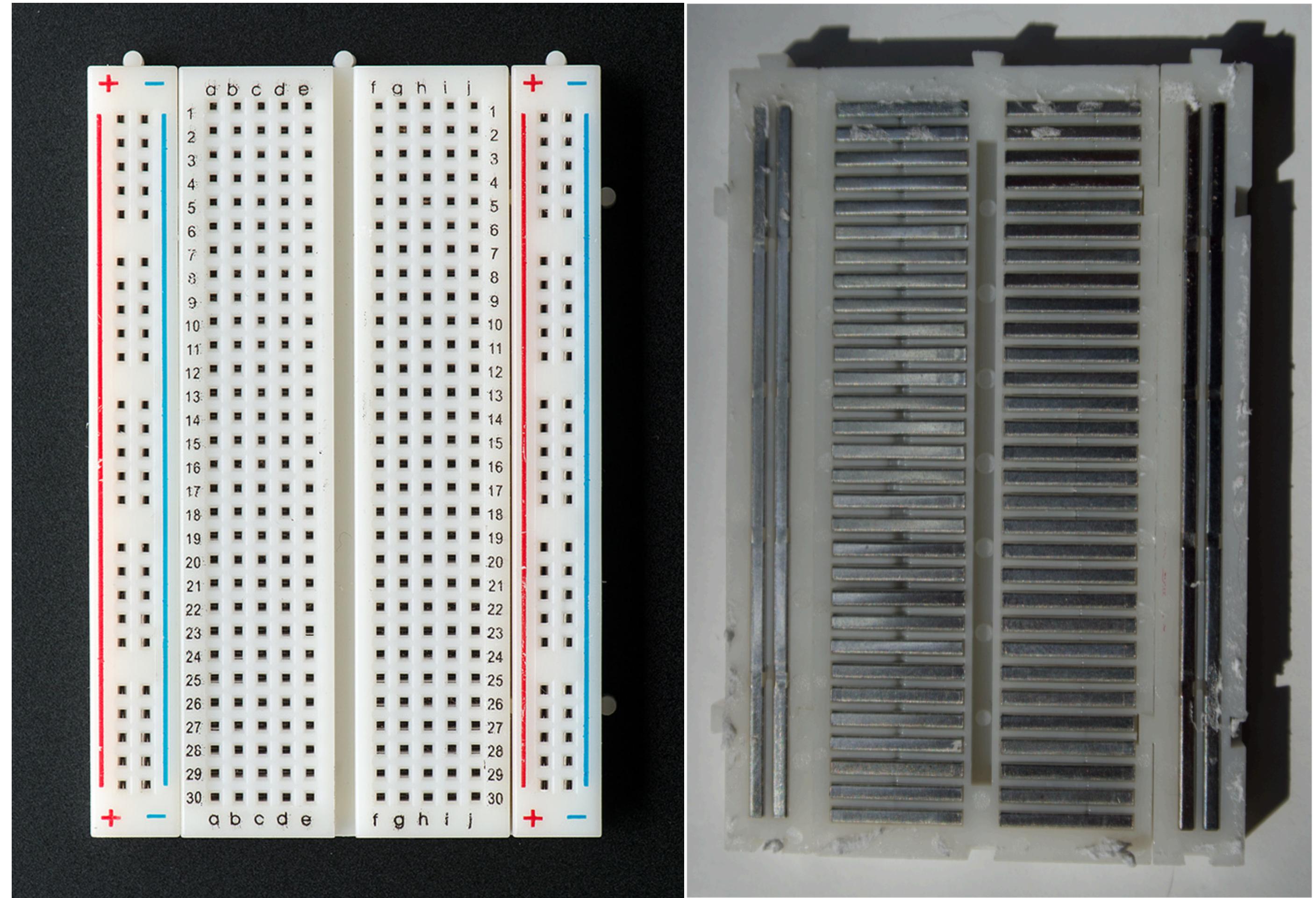
- ▶ We will build our circuits on breadboards and power them with 9V batteries




BREADBOARDS

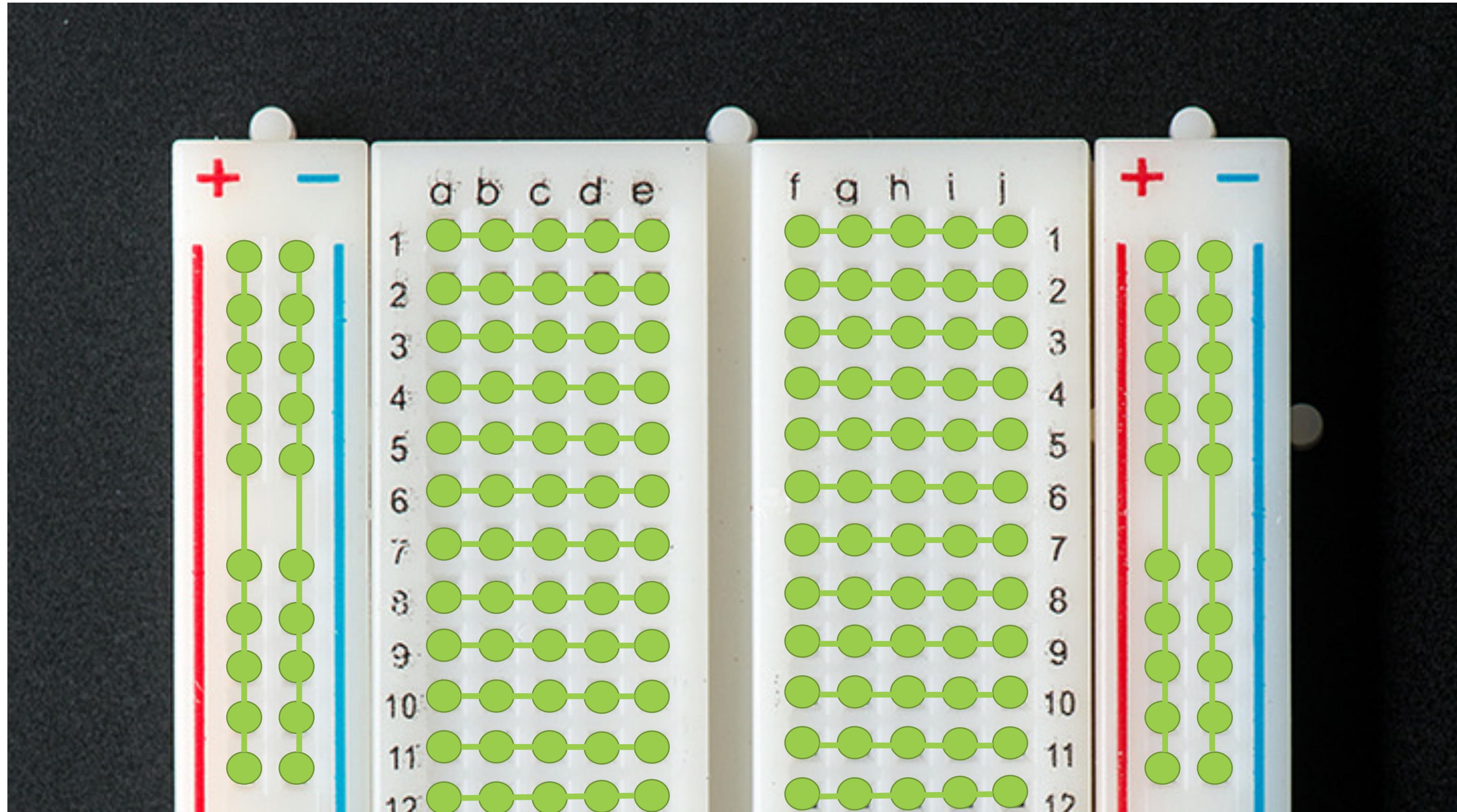

BREADBOARDS

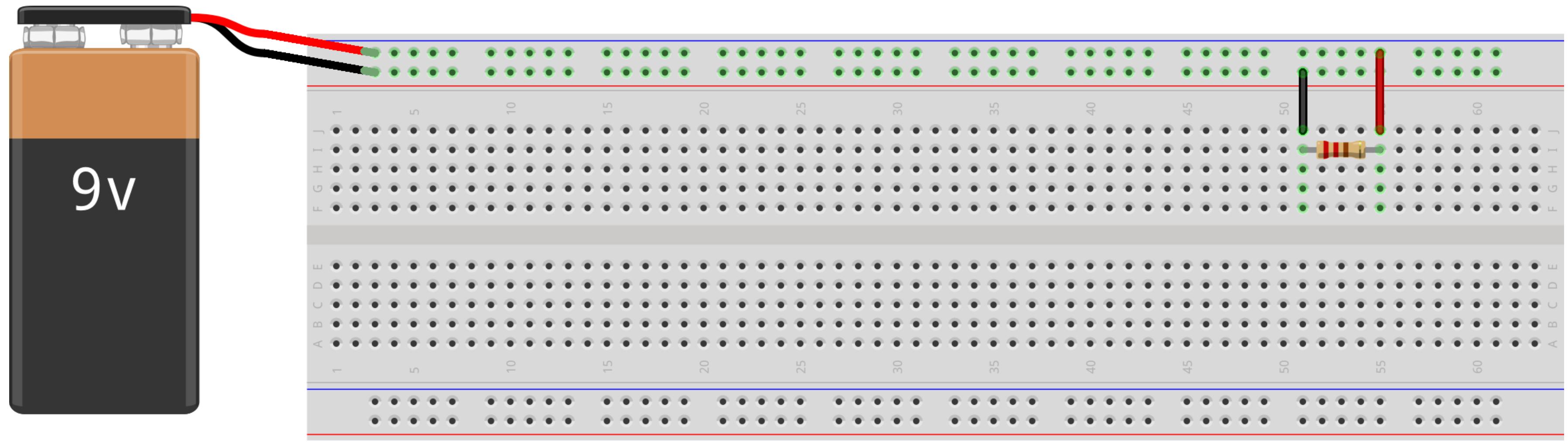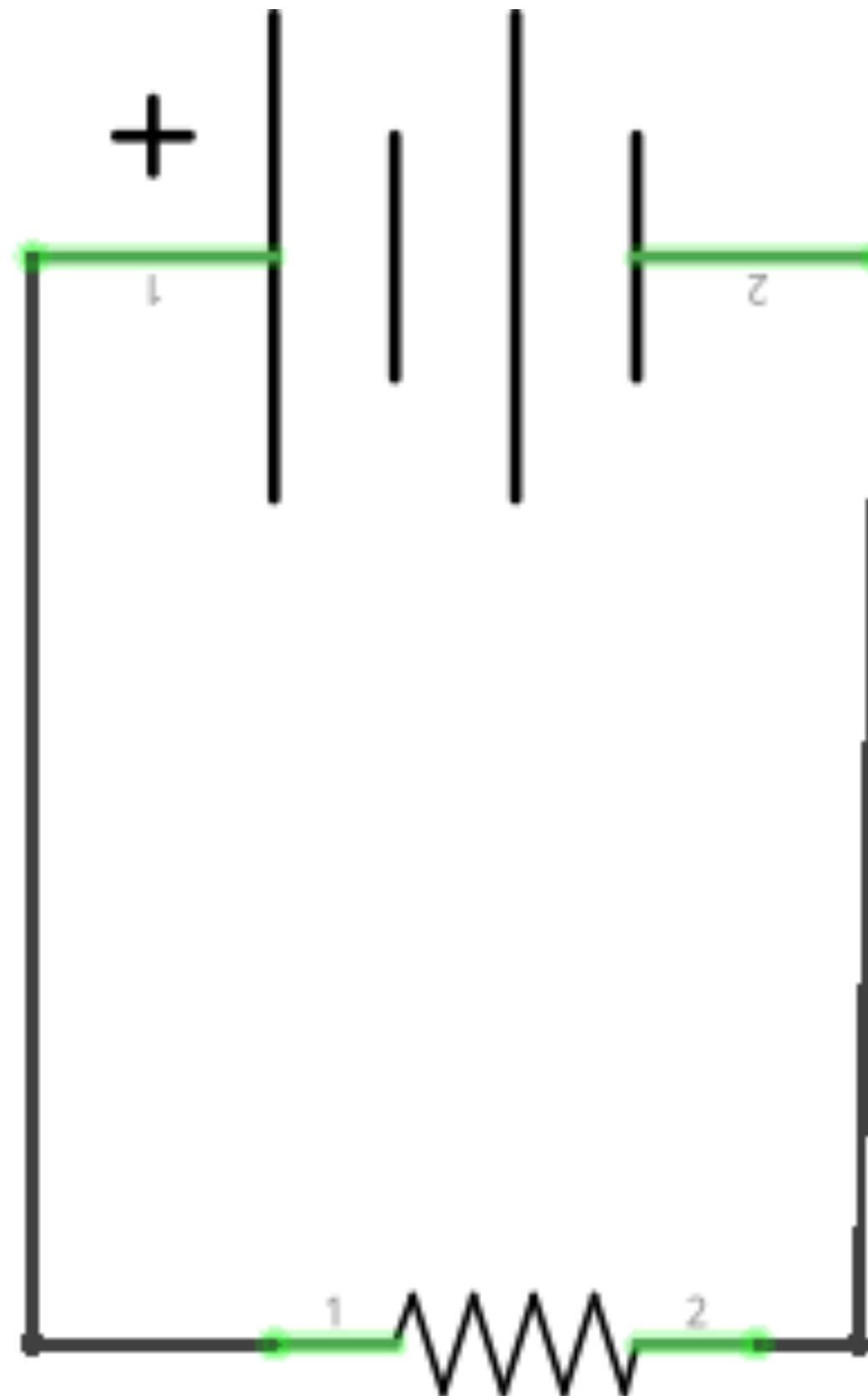


BREADBOARDS

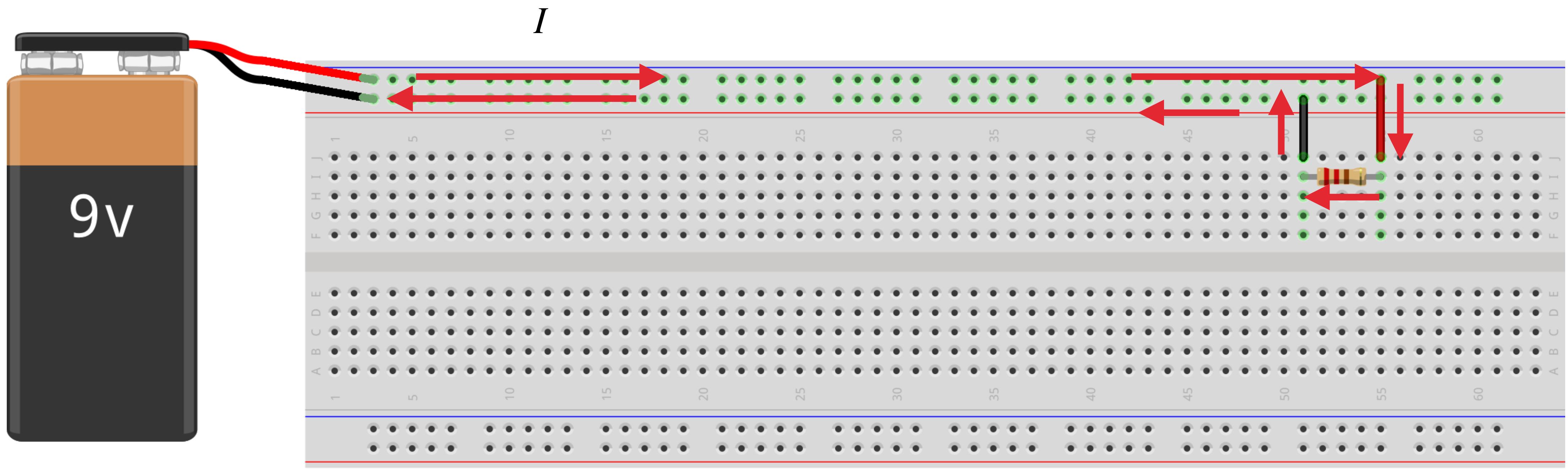


fritzing

BREADBOARDS

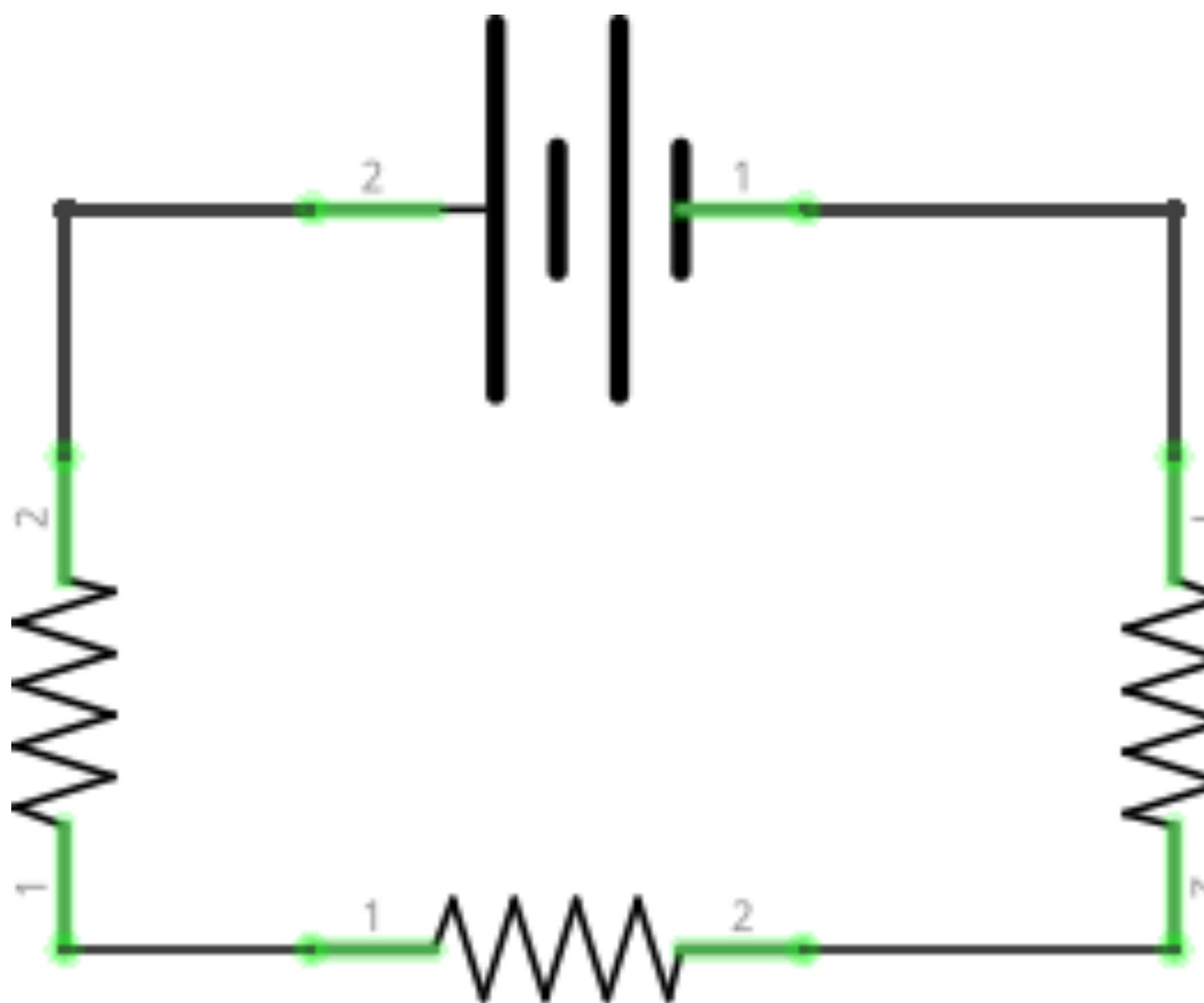


BREADBOARDS

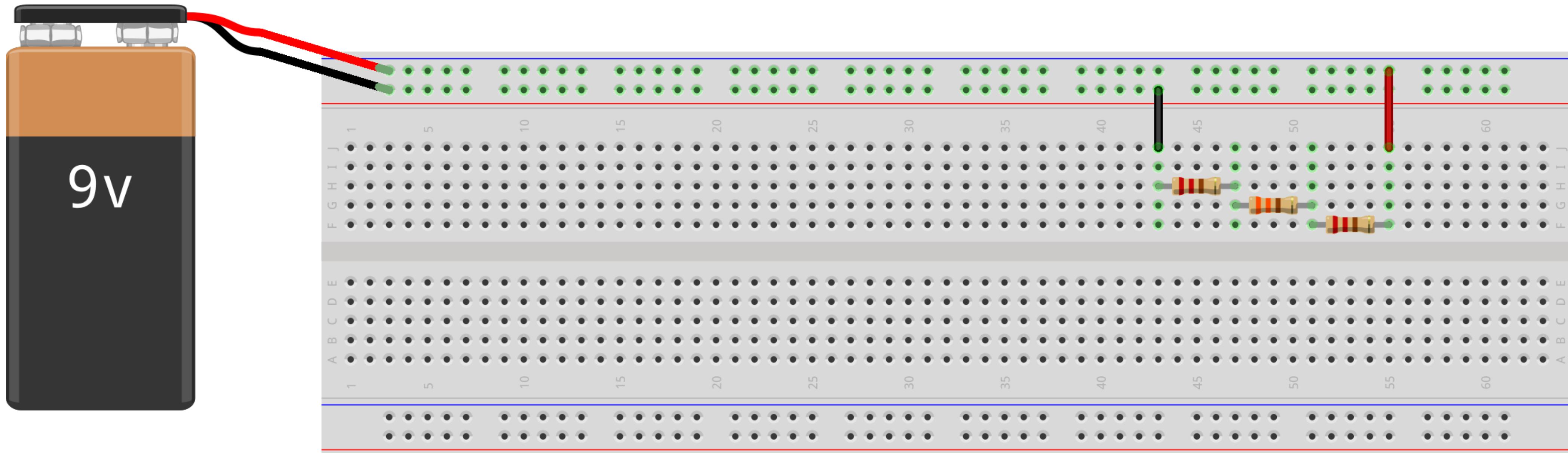


fritzing

BREADBOARDS

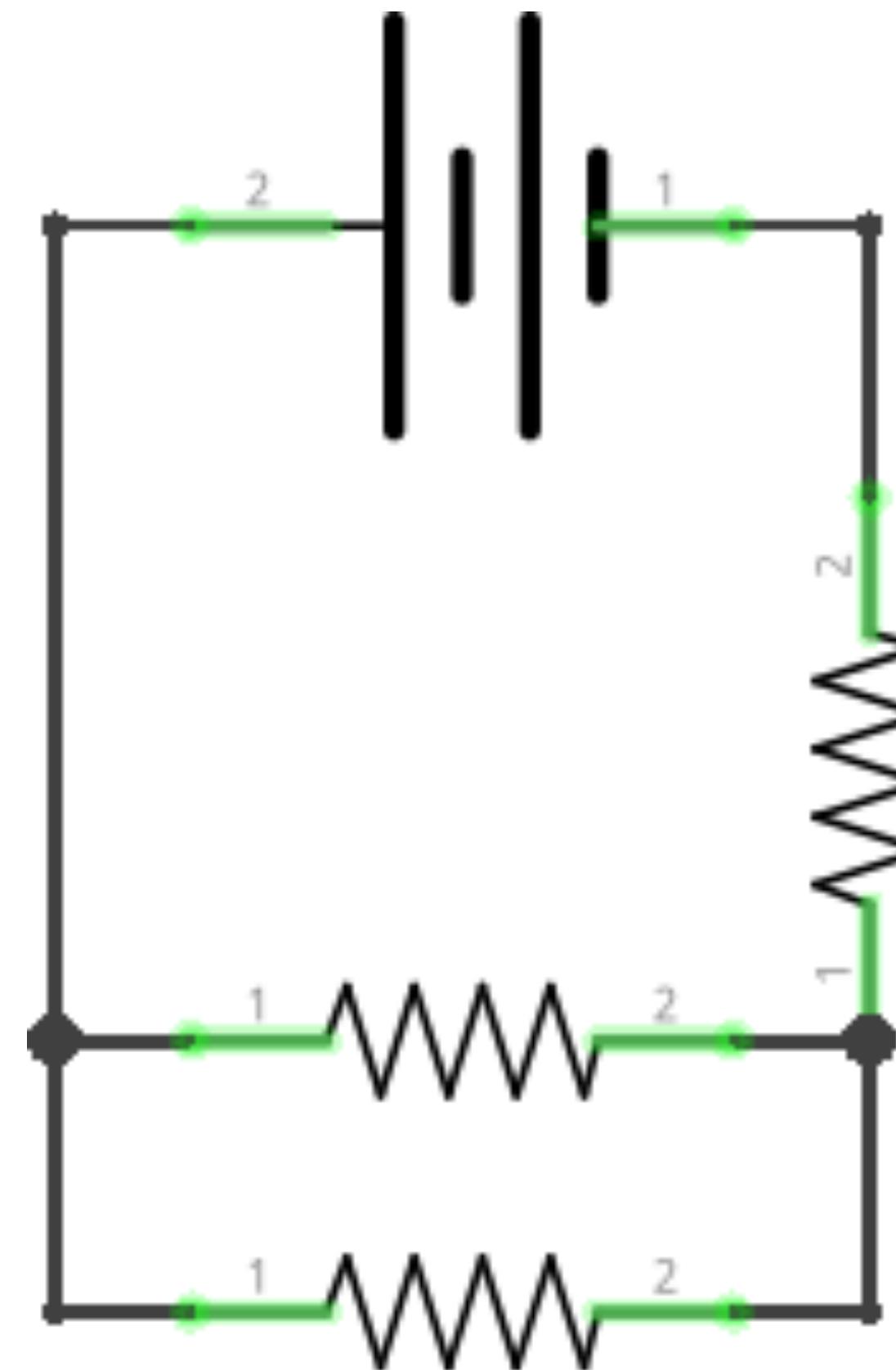


BREADBOARDS

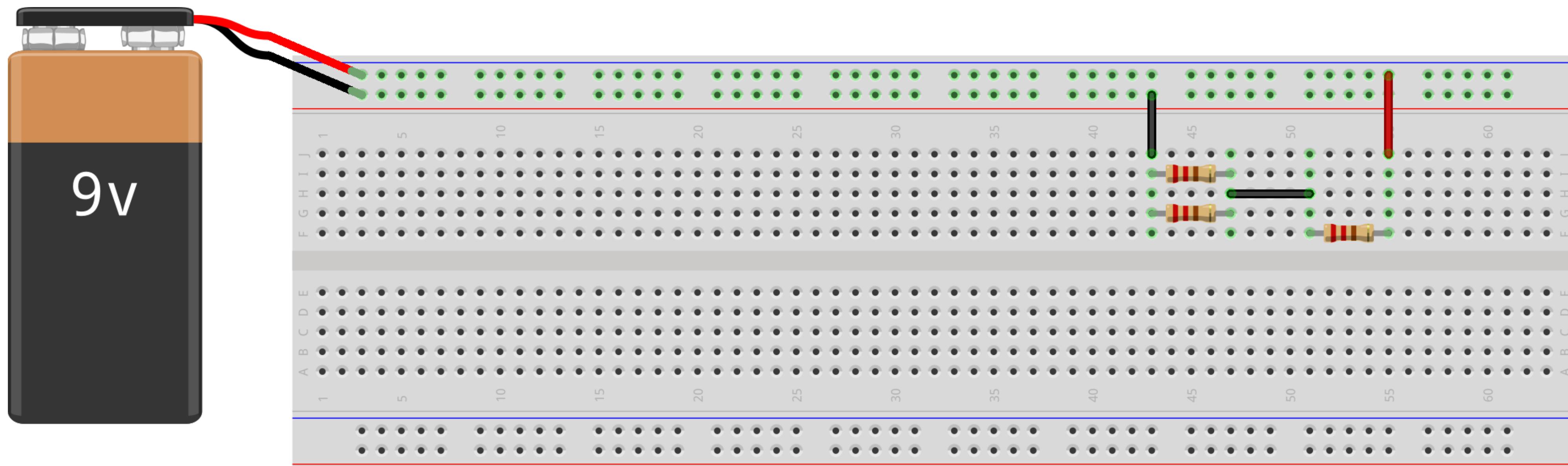


fritzing

BREADBO



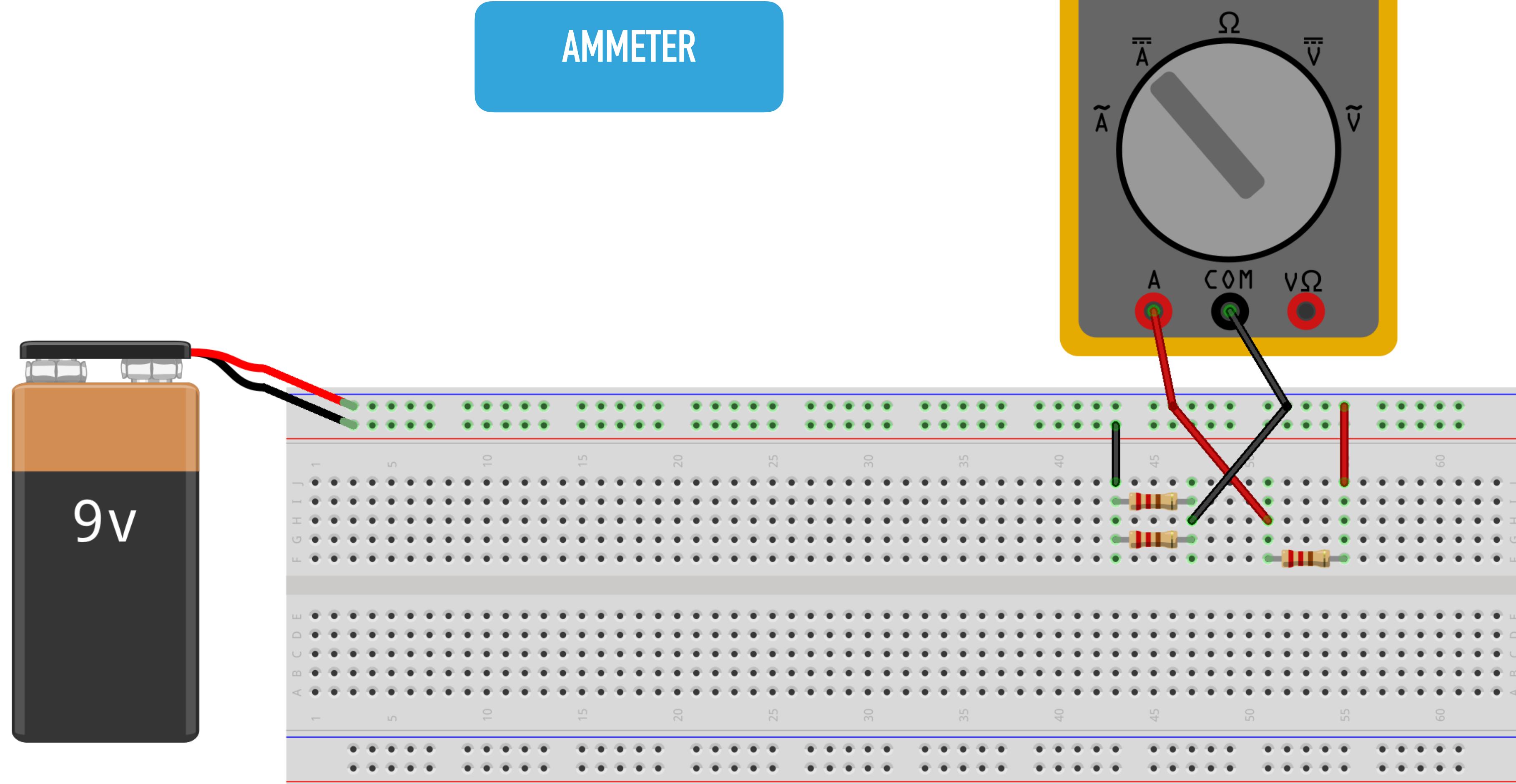





fritzing

BREADBOARD



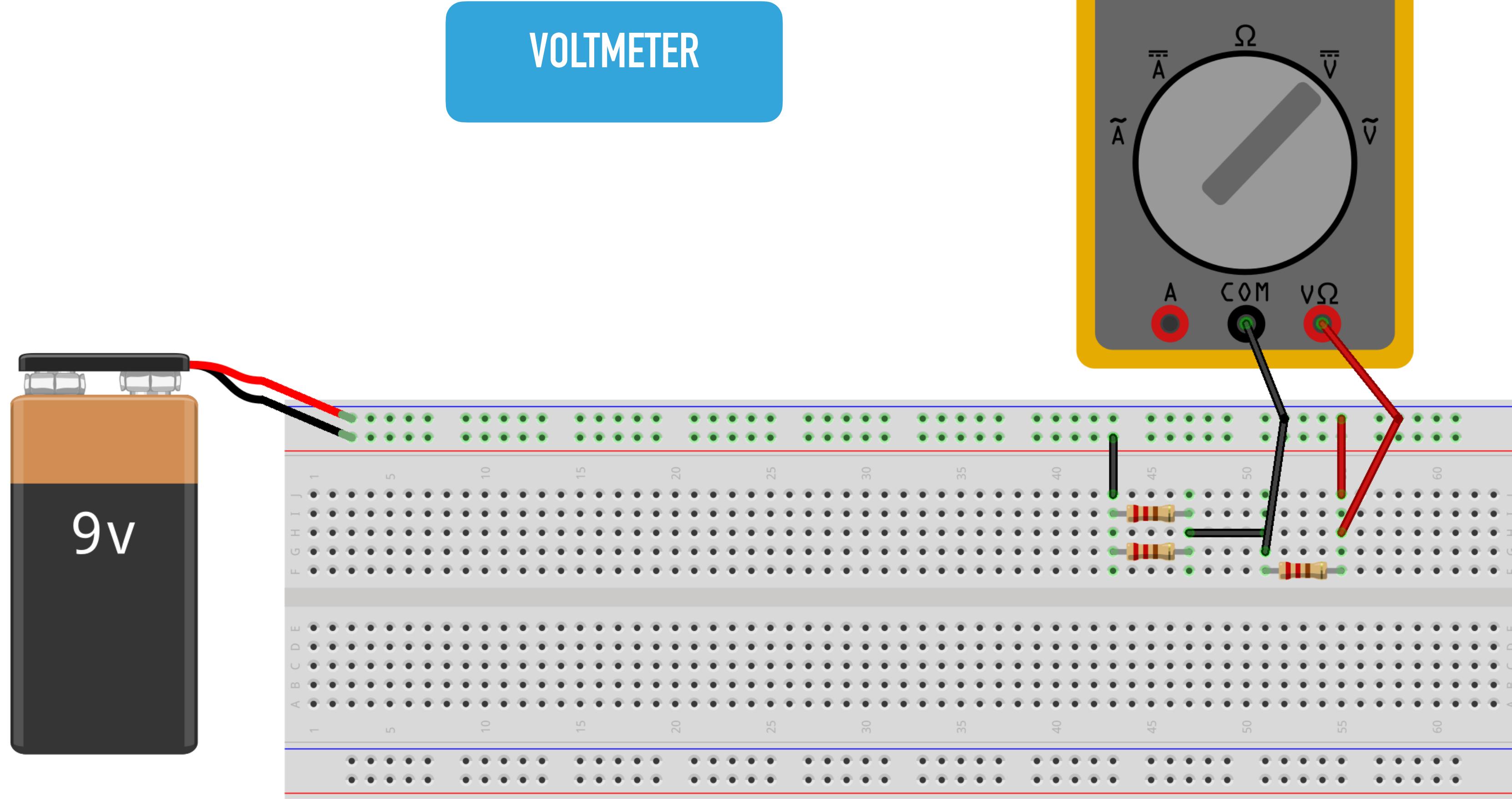


fritzing

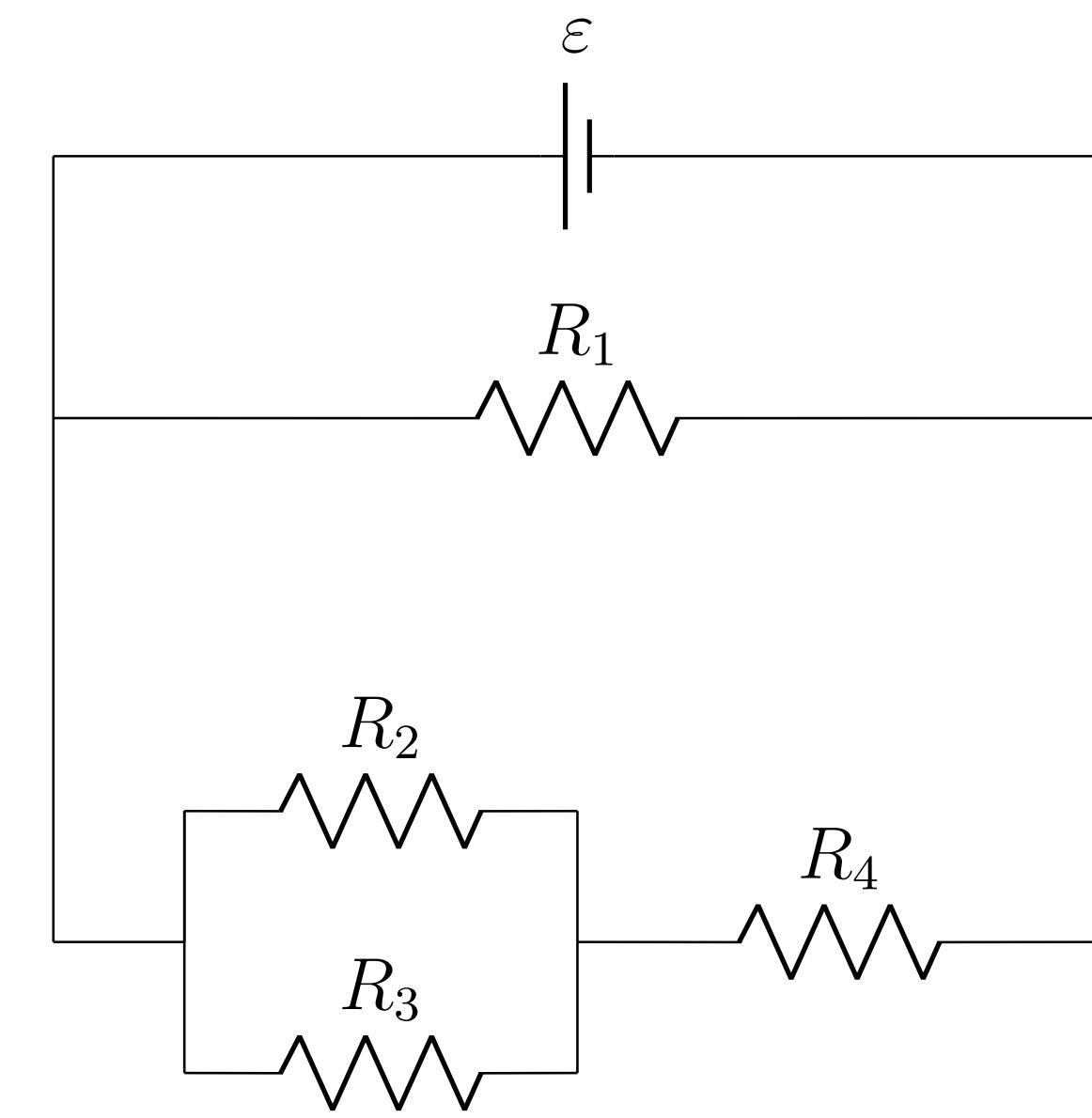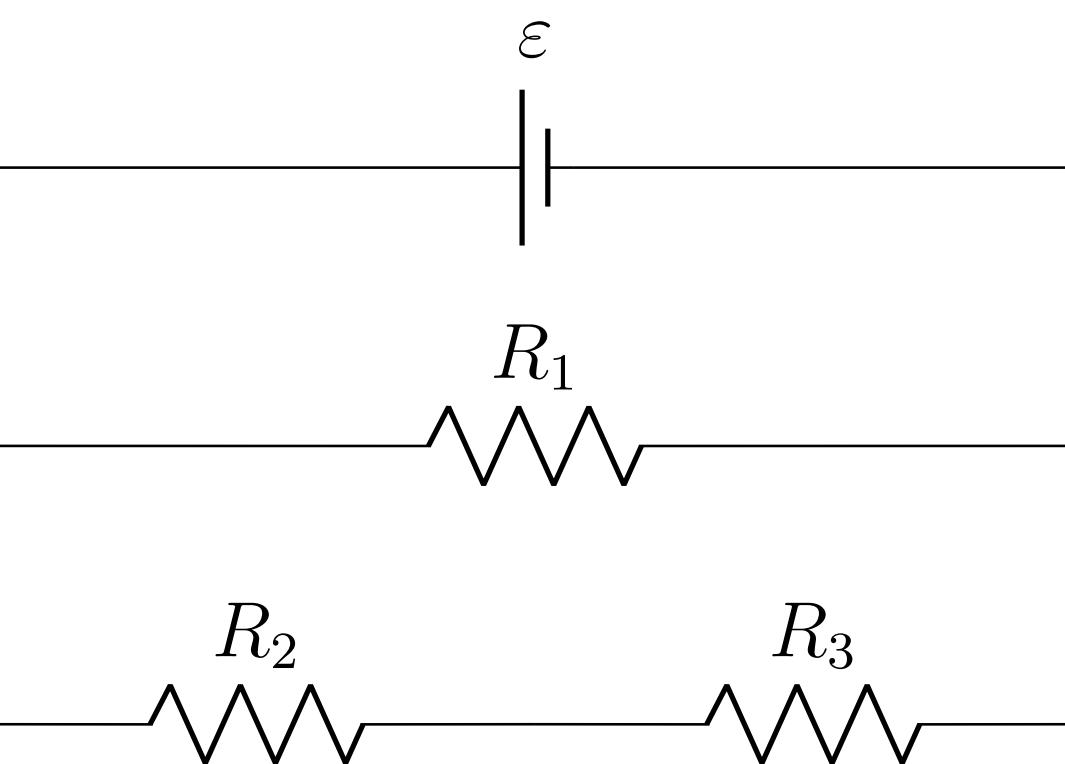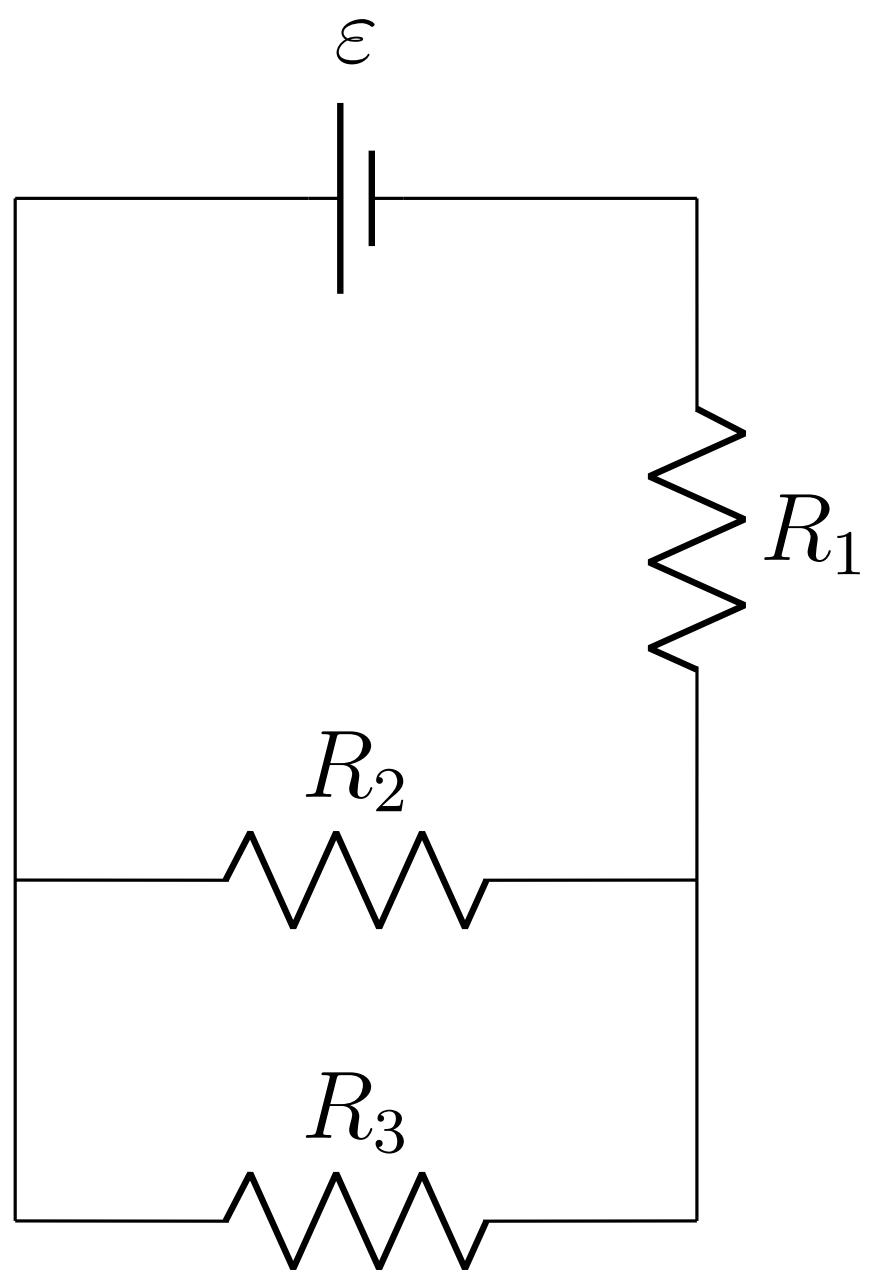

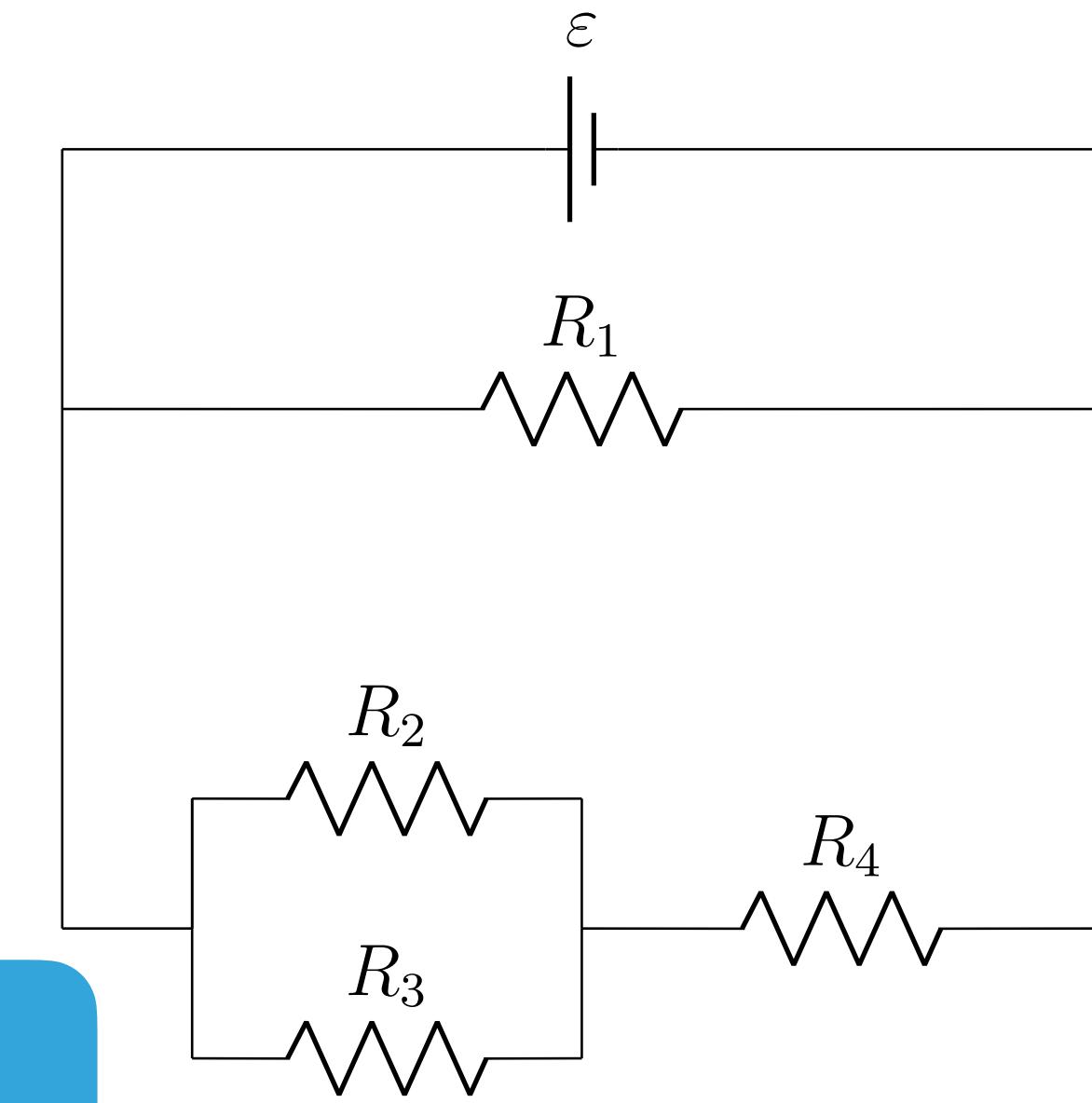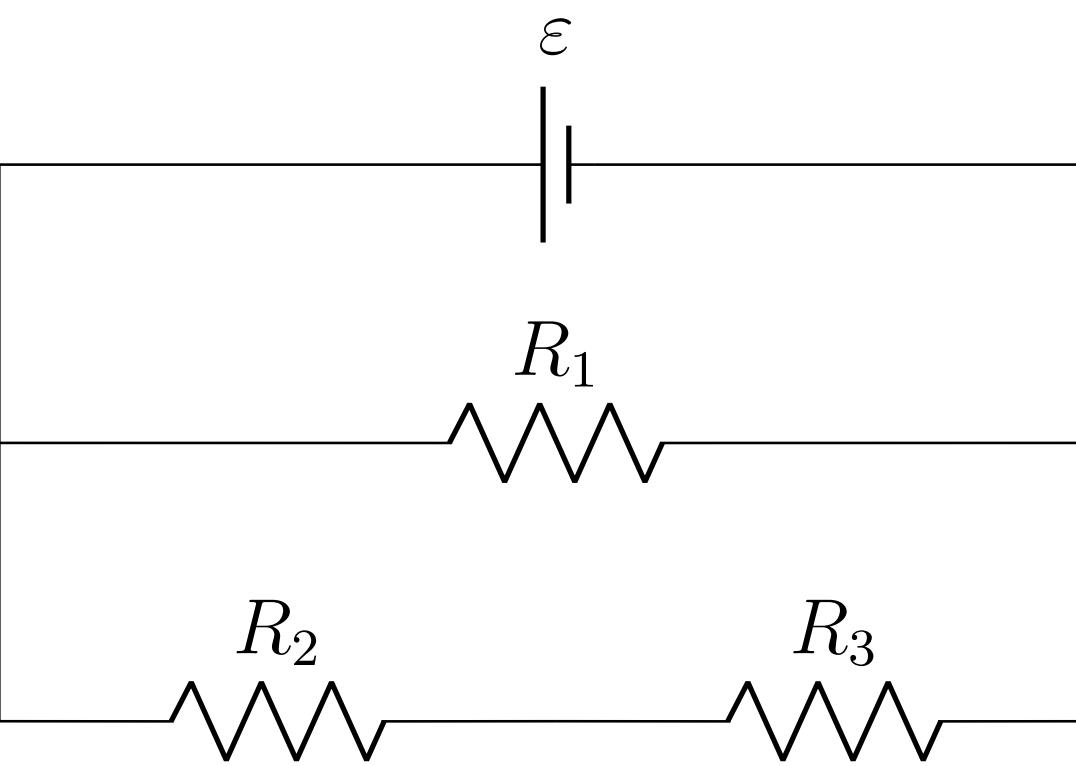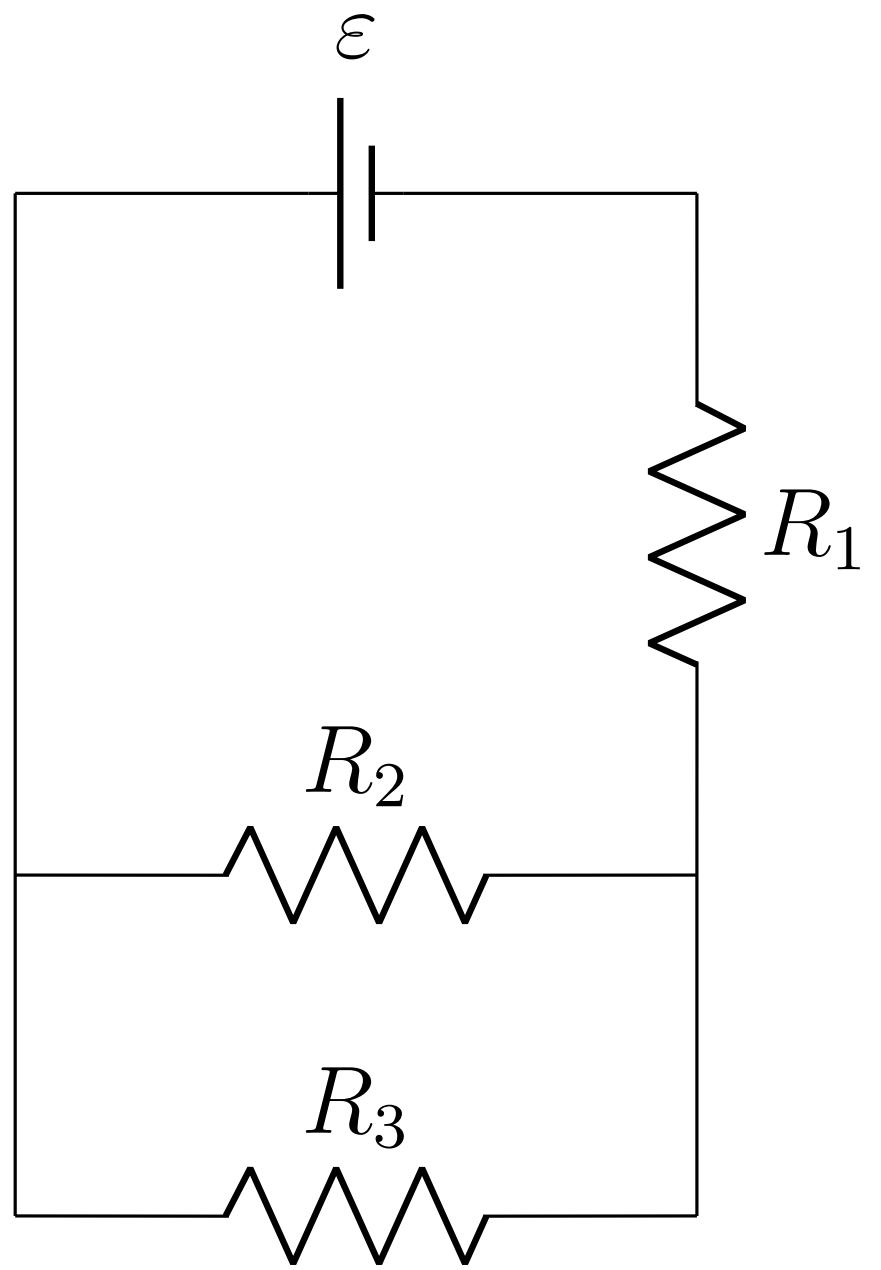

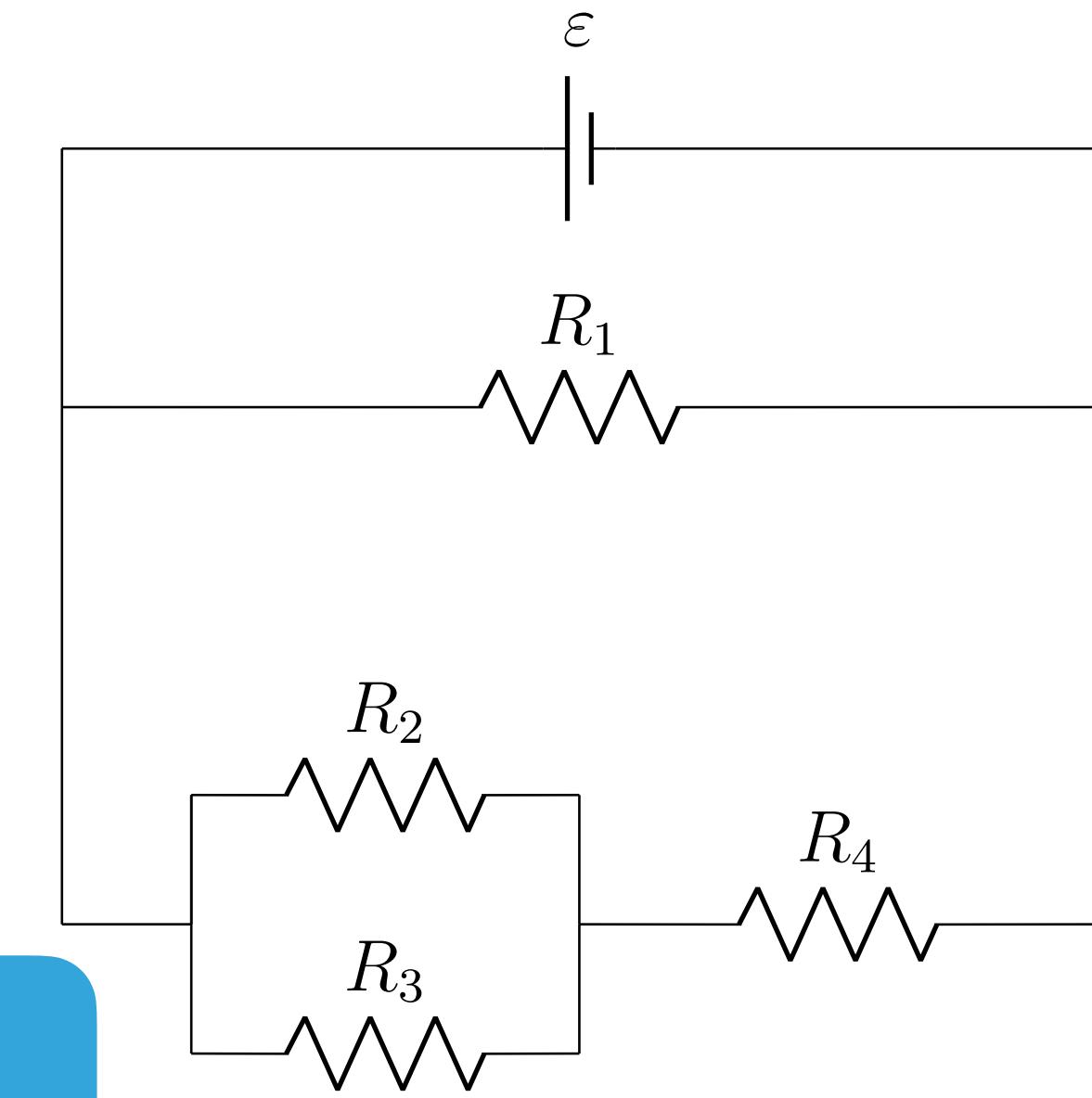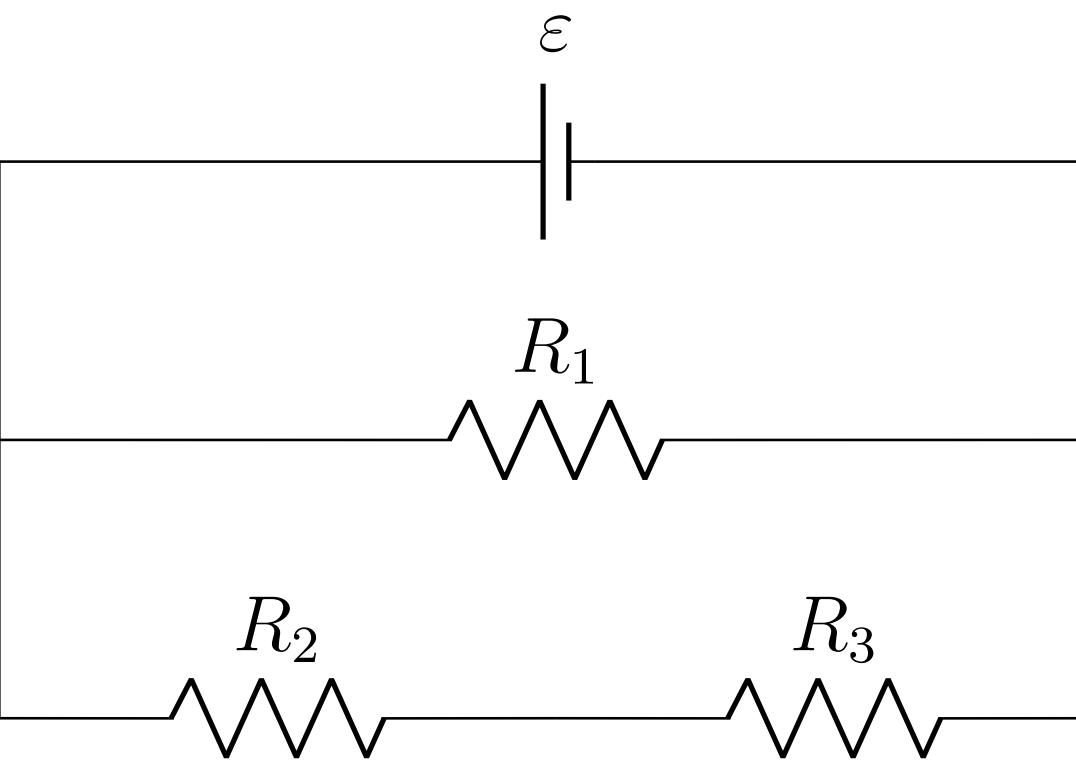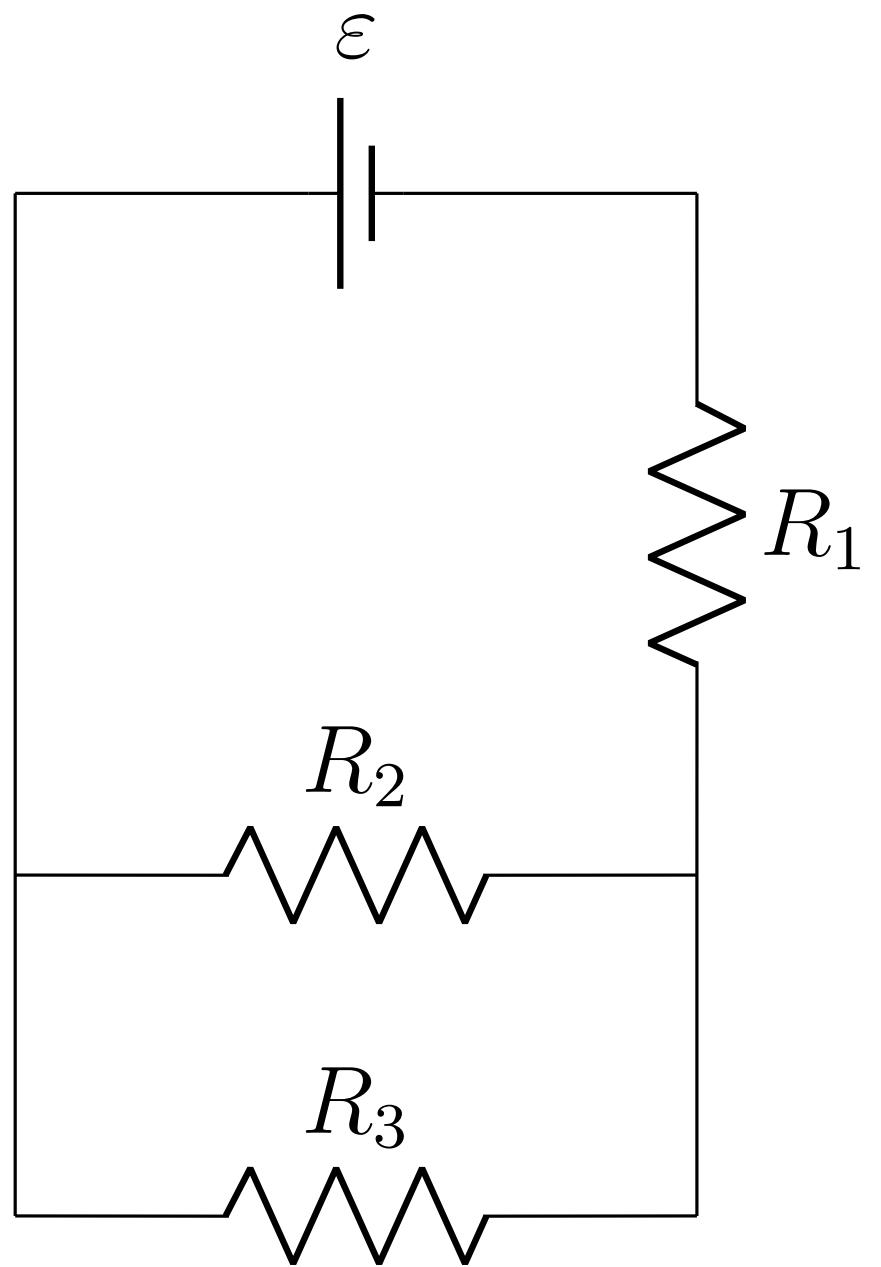First predict, then measure, current through and voltage across each resistor




You can choose the values for your resistors

UNCERTAINTY

Uncertainty of predicted values:

- ▶ You will measure ε and its uncertainty $\Delta\varepsilon$ (more on this in a second)
- ▶ Each resistor has a tolerance value which is the uncertainty of its resistance
- ▶ These uncertainties propagate to form the uncertainty in the predicted values of I and ΔV


EXAMPLE

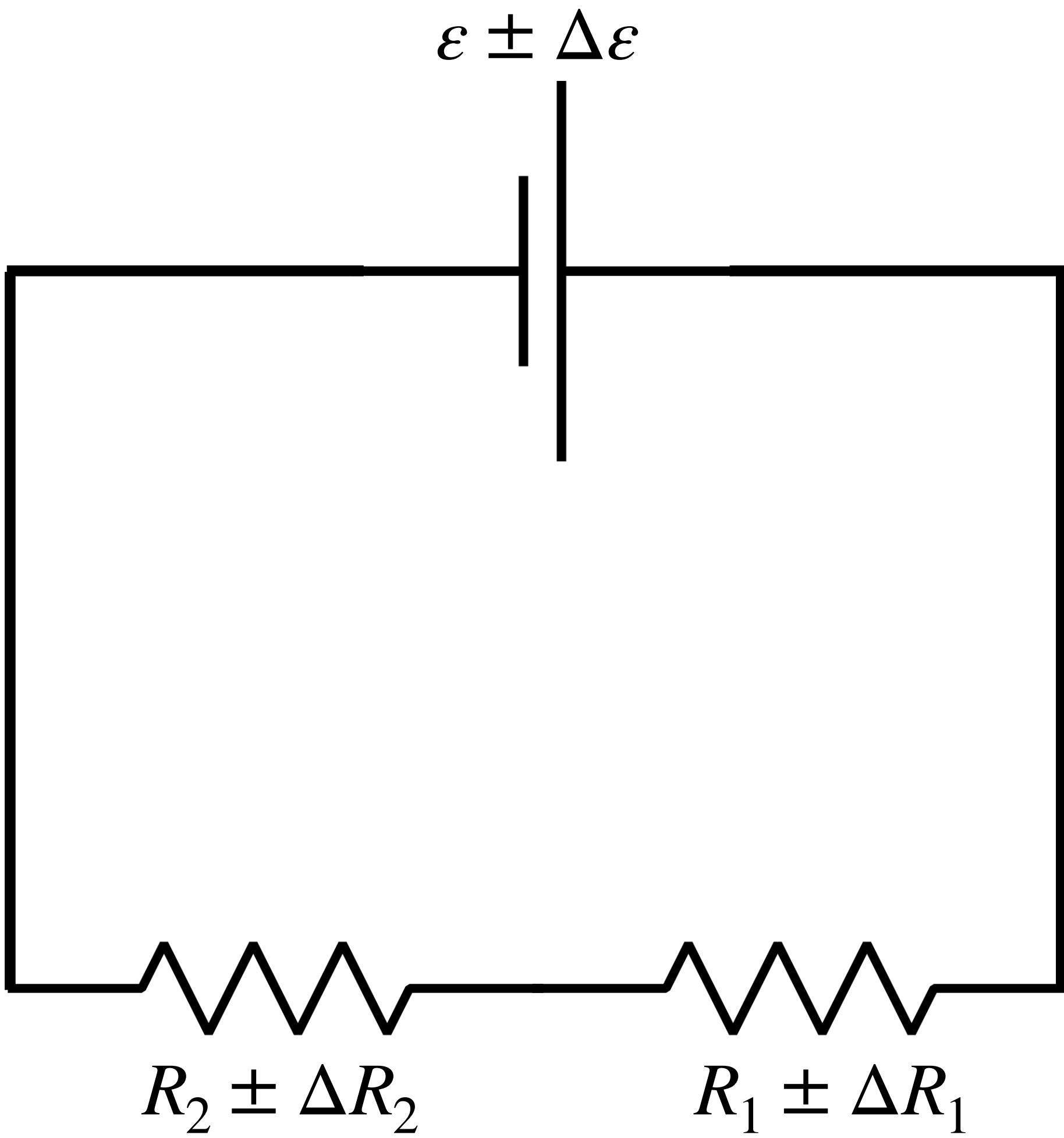

EXAMPLE

If a resistor with resistance R has tolerance of 10%, then

$$\Delta R = 0.1 \cdot R$$

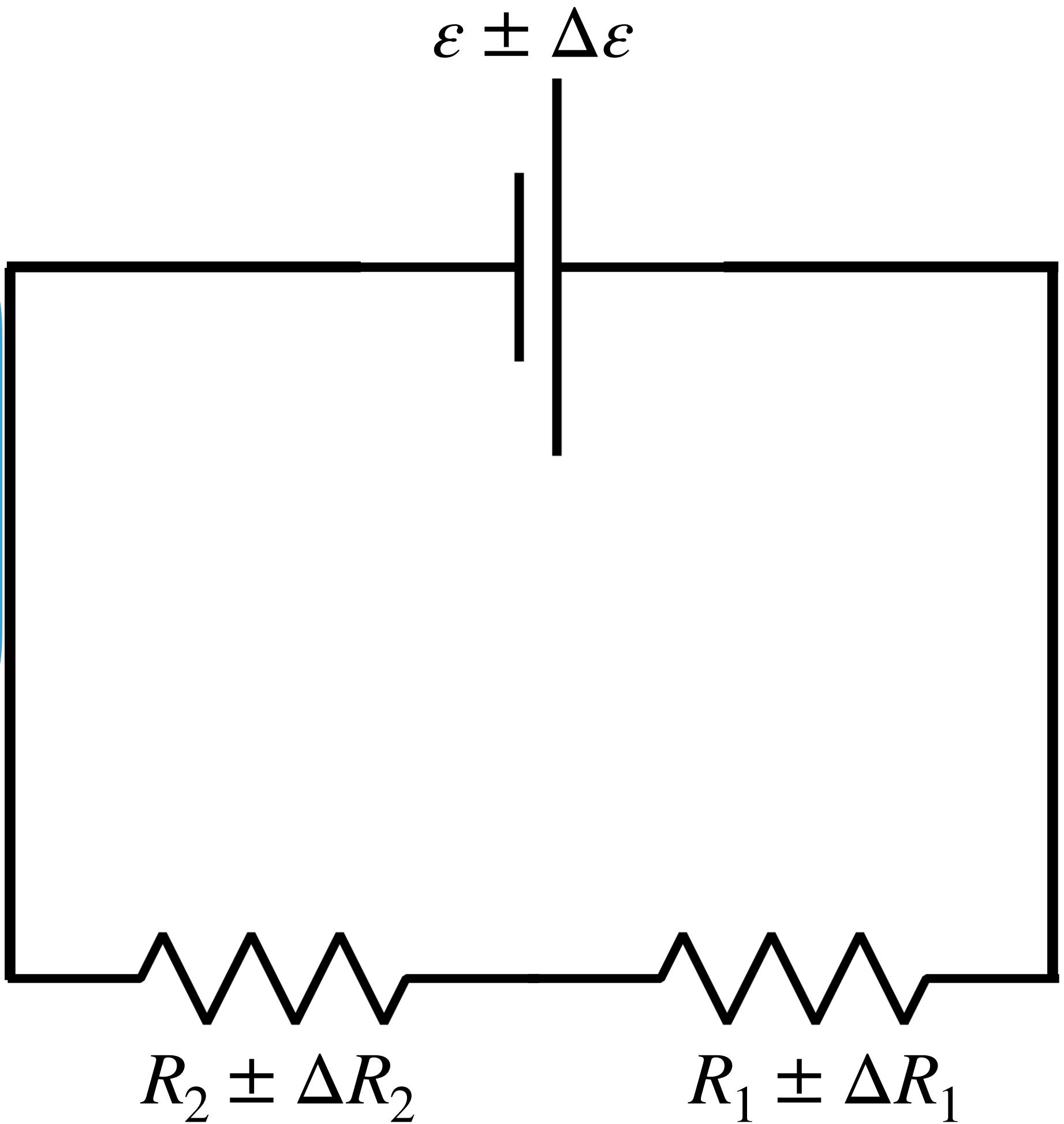


EXAMPLE

$$I_{\text{pred}} = \frac{\varepsilon}{R_1 + R_2} = \frac{\varepsilon}{R_{\text{tot}}}$$

$$R_{\text{tot}} = R_1 + R_2, \quad \Delta R_{\text{tot}} = \sqrt{\Delta R_1^2 + \Delta R_2^2}$$

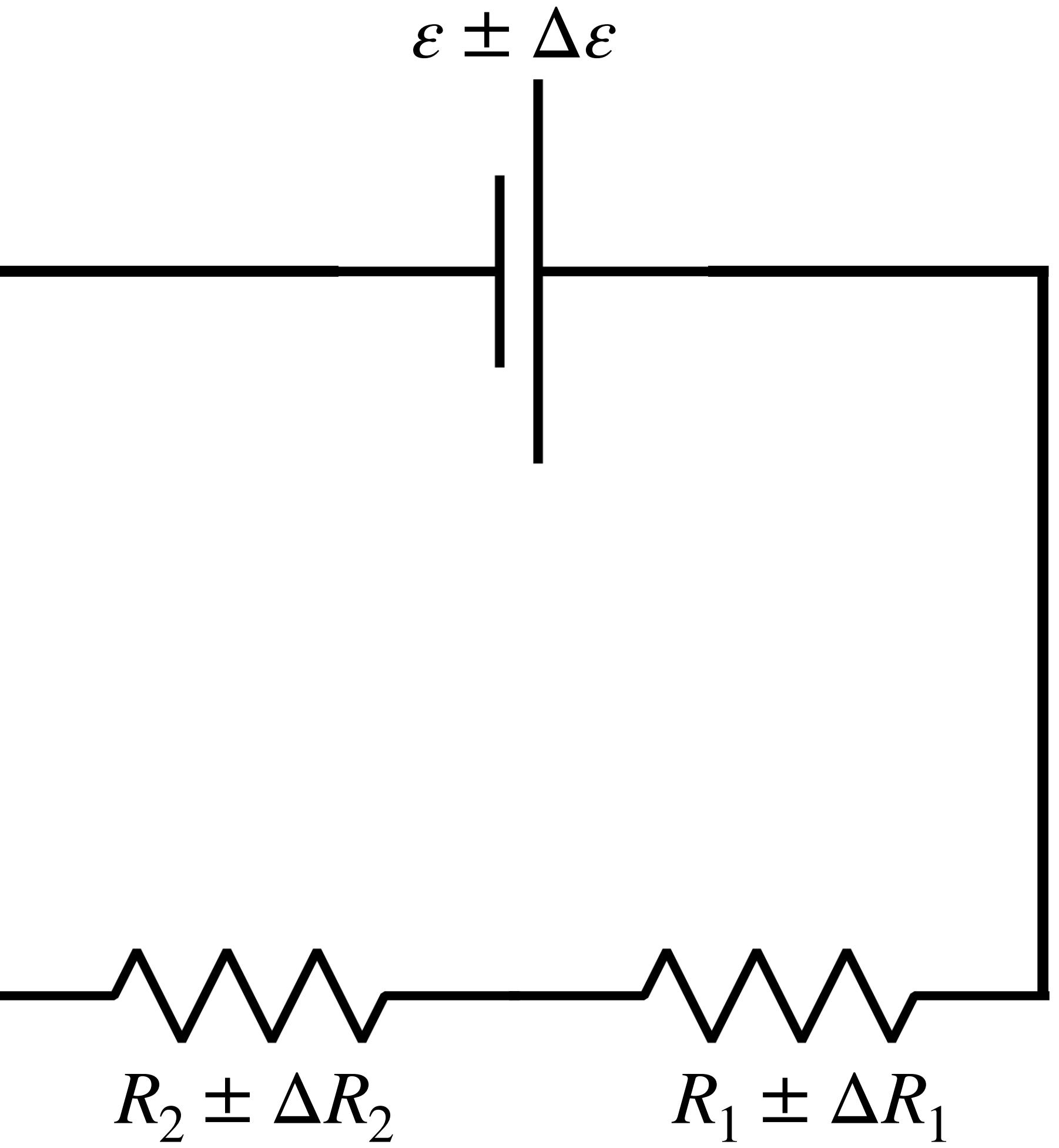
$$\Delta I_{\text{pred}} = \frac{\varepsilon}{R_{\text{tot}}} \sqrt{\left(\frac{\Delta R_{\text{tot}}}{R_{\text{tot}}} \right)^2 + \left(\frac{\Delta \varepsilon}{\varepsilon} \right)^2}$$



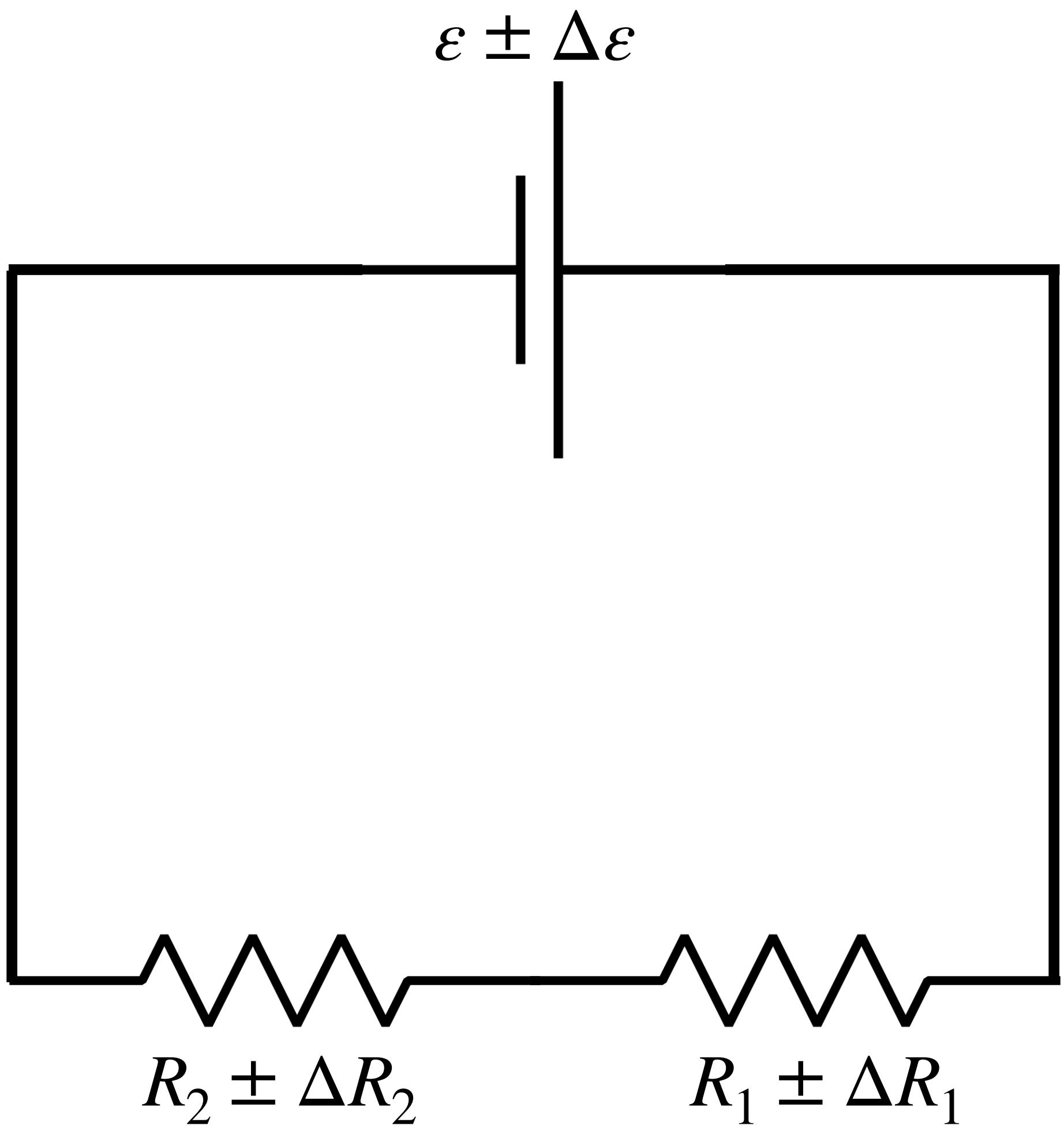EXAMPLE

$$V_{1,\text{pred}} = I_{\text{pred}} \cdot R_1$$

$$\Delta V_{1,\text{pred}} = \Delta I_{\text{pred}} \cdot R_1 \sqrt{\left(\frac{\Delta I_{\text{pred}}}{I_{\text{pred}}}\right)^2 + \left(\frac{\Delta R_1}{R_1}\right)^2}$$



UNCERTAINTY

- ▶ Your values and uncertainties from your measured quantities are the mean and standard deviation from the multimeter

DATA TABLE FOR PART 1

				Predicted Values				Measured Values			
Circuit	Resistor #	R	R Tol.	I_{pred}	ΔI_{pred}	V_{pred}	ΔV_{pred}	I_{meas}	ΔI_{meas}	V_{meas}	ΔV_{meas}
0	1										
1	1										
	2										
	3										
2	1										
	2										
	3										
3	1										
	2										
	3										
	4										

Table 1: Data Table for Part 1

CALCULATIONS AND UNCERTAINTIES

- ▶ With several resistors, the uncertainty calculations can get a bit rough
- ▶ You will use Python's [uncertainties](#) module to help you

DETERMINING THE BATTERY PROPERTIES

- ▶ Before you begin the main part of the lab, you must determine both the **emf** and the **internal resistance** of the battery
 - ▶ You will use both of these values for your predictions later on in the lab!

DETERMINING THE BATTERY PROPERTIES

- ▶ It is up to you to devise an experiment (or set of experiments) that will enable you to determine ε , $\Delta\varepsilon$, r_{int} , and Δr_{int}
- ▶ You can make as many measurements as you like, and use any resistors you want