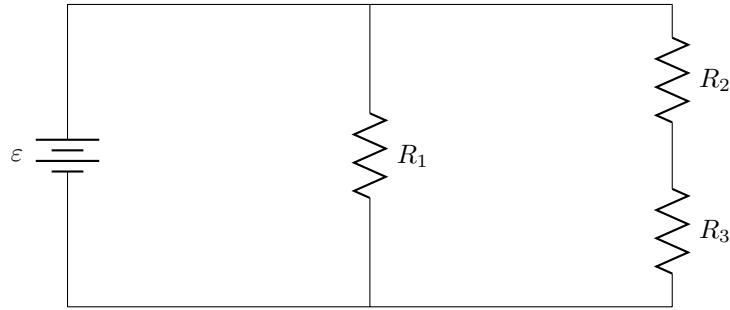


## Quiz 6

In the following diagram:  $R_1 = 10\ \Omega$ ,  $R_2 = 10\ \Omega$ , and  $R_3 = 5\ \Omega$ . The battery emf  $\varepsilon = 3.0\ \text{V}$ .



1. Find the currents  $I_1, I_2, I_3$  through each resistor
2. Find the potential difference  $\Delta V$  across each resistor
3. Find the power dissipated through each resistor