

Quiz 7


The following information may or may not be of use:

$$\text{Ohm's Law: } I = \frac{\Delta V}{R}$$

$$\text{Electrical Resistance: } R = \frac{L}{\sigma A}$$

$$\text{Power: } P = I\Delta V$$

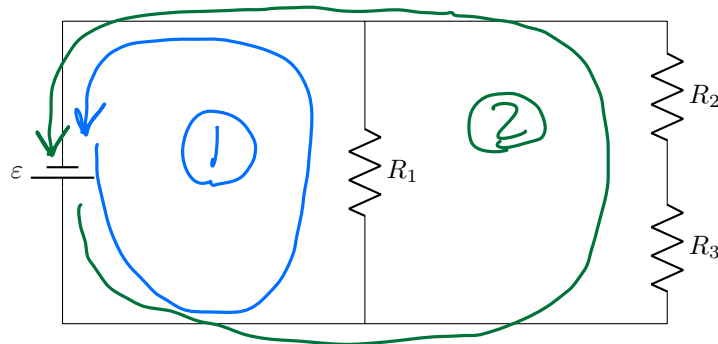In the following diagram: $R_1 = 100 \, \Omega$, $R_2 = 100 \, \Omega$, and $R_3 = 220 \, \Omega$. The battery emf $\varepsilon = 3.0 \, \text{V}$.



1. Find the currents I_1, I_2, I_3 through each resistor
2. What is the power output of the battery?

Loop rule. 2 eqns.

$$\textcircled{1} \quad \varepsilon - I_1 R_1 = 0$$

$$\textcircled{2} \quad \varepsilon - I_2 R_2 - I_3 R_3 = 0$$

$$I_2 = I_3, \text{ since } R_2 \text{ \& } R_3 \text{ are in } \underline{\text{series}}$$

$$\text{Node Rule: } I_{\text{batt}} = I_1 + I_2$$

$$\textcircled{1} \rightarrow I_1 = \frac{\mathcal{E}}{R_1} = \frac{3 \text{ V}}{100 \Omega}$$

$$\boxed{I_1 = 0.03 \text{ A}}$$

$$\textcircled{2} \rightarrow \mathcal{E} - I_2 R_2 - I_2 R_3 = 0$$

$$I_2 = \frac{\mathcal{E}}{R_2 + R_3} = \frac{3 \text{ V}}{320 \Omega}$$

$$I_2 = I_3 = 0.0094 \text{ A}$$

$$P_{\text{batt}} = I_{\text{batt}} \Delta V_{\text{batt}} = I_{\text{batt}} \mathcal{E}$$

$$I_{\text{batt}} = I_1 + I_2 = 0.039 \text{ A}$$

$$P_{\text{batt}} = (0.039 \text{ A})(3 \text{ V}) = 0.118 \text{ W}$$