

Purpose

In this lab you will build a very simple circuit and use it to predict and measure the conductive properties of wires of different lengths and sizes.

Introduction

Nichrome (NiCr) is a metal alloy of nickel and chromium with a very low electron mobility. The properties of Nichrome are shown in Table 1.

In this lab, you will apply a voltage to Nichrome wires of different thicknesses and lengths. To get wires of different lengths, you will simply attach clip leads at different locations along the wires – you will not cut the wires.

Property	Value
Electron density (n)	$9 \times 10^{28} \text{ m}^{-3}$
Electron mobility (u)	$7 \times 10^{-5} \frac{\text{m/s}}{\text{N/C}}$
Charge carrier	electron

Table 1

Procedure

The Connecting Wires

The purpose of this lab is to investigate the affect that different lengths and thicknesses of nichrome wires has on the current flowing through the circuit. Normally, we can ignore the connecting wires in circuits, but the nichrome has similar conductive properties as the connecting wires. In the first part of the lab, we will measure the conductive properties of the connecting wires in order to isolate the affect of nichrome later on the lab.

1. Begin by connecting the two leads of the power supply through an ammeter, with nothing else connected. (Do not turn on the power supply; have your instructor approve the circuit).
2. The loop equation for this circuit is

$$\varepsilon - E_1 L_1 - E_2 L_2 - E_3 L_3 - E_4 L_4 = 0$$

We can use the electron current relation $i = nAuE$ to rewrite the loop equation:

$$\varepsilon - \frac{iL_1}{n_1 A_1 u_1} - \frac{iL_2}{n_2 A_2 u_2} - \frac{iL_3}{n_3 A_3 u_3} - \frac{iL_4}{n_4 A_4 u_4} = 0$$

Or

$$\varepsilon - \left(\frac{L_1}{n_1 A_1 u_1} + \frac{L_2}{n_2 A_2 u_2} + \frac{L_3}{n_3 A_3 u_3} + \frac{L_4}{n_4 A_4 u_4} \right) i = 0 \quad (1)$$

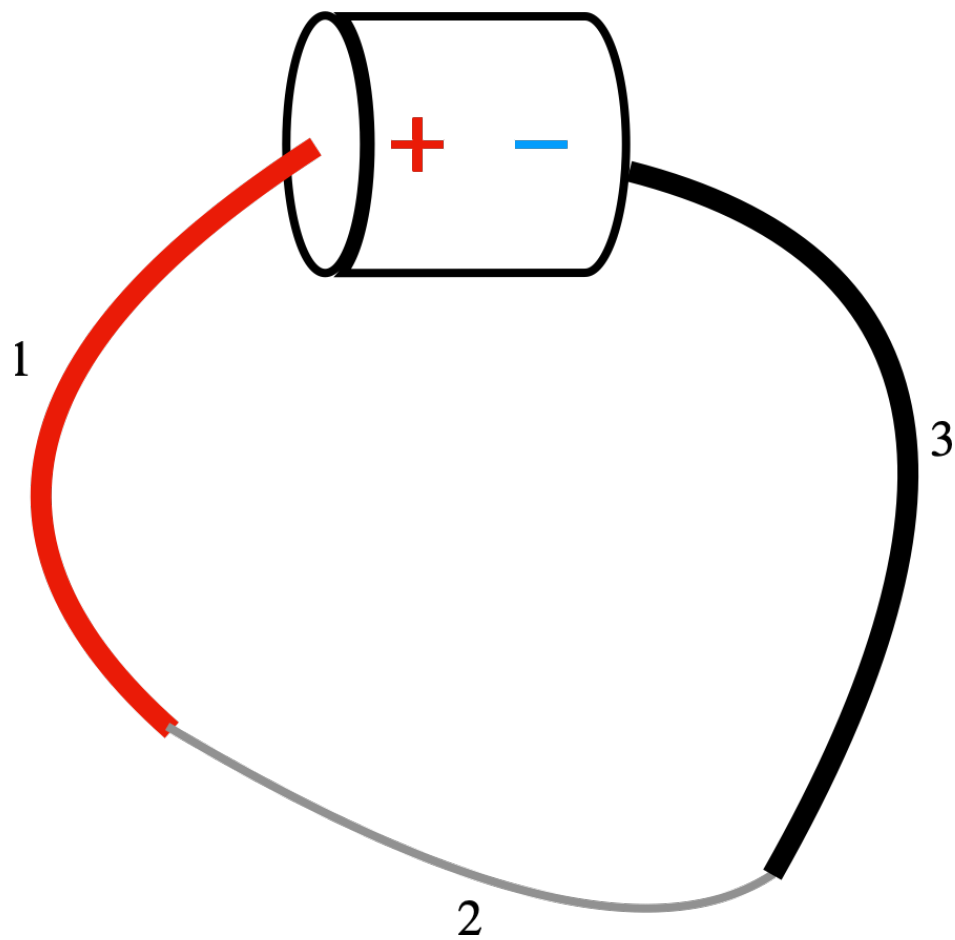


Figure 1

The term $\frac{L_1}{n_1 A_1 u_1} + \frac{L_2}{n_2 A_2 u_2} + \frac{L_3}{n_3 A_3 u_3} + \frac{L_4}{n_4 A_4 u_4}$ will appear in our loop equations later on. We don't need to know the individual values, we only need the sum. We can obtain a number for this term by connecting the circuit to a known voltage ε and measuring the resulting current i .

3. Turn on the power supply at a low voltage, around 0.5 V, and measure the current. The multimeter calculates the mean of many current measurements automatically. Use the mean and standard deviation for your measurement and uncertainty.
4. Now you can use Equation 1 to solve for $\frac{L_1}{n_1 A_1 u_1} + \frac{L_2}{n_2 A_2 u_2} + \frac{L_3}{n_3 A_3 u_3} + \frac{L_4}{n_4 A_4 u_4}$. We will call this term r_{wires} , since it looks very much like a resistor. Equation 1 then becomes $\varepsilon - i r_{\text{wires}} = 0$; solving for r_{wires} gives: $r_{\text{wires}} = \frac{\varepsilon}{i}$. Record this result for later use. Your current measurement should have included an uncertainty, therefore your value for r_{wires} will also have an uncertainty. If the uncertainty of I is ΔI , then the uncertainty for i is $\Delta i = \Delta I / 1.6 \times 10^{-19} \text{ C}$. The uncertainty for r_{wires} is then $\Delta r_{\text{wires}} = \frac{\varepsilon}{i} \frac{\Delta i}{i}$.

Important: Measuring Current

When the multimeter is on, a live-updating estimate of the current is shown on the screen. Towards the bottom of the screen, the meter automatically keeps track of some statistics for you. You will use these for your current measurement.

1. When you are ready to measure current, press the DC I button (this is important as it refreshes the statistics).
2. The multimeter continually measures the current and calculates the mean and standard deviation for you. Wait until there are at least 10 measurements, then record these values. The mean is your estimate for the value of the current, the standard deviation is your estimate for the uncertainty.

Investigating the Nichrome Wire

Now that we have quantified the effect of the connecting wires, we can play with the Nichrome.

1. At your lab station are two pieces of nichrome wire, one thick ($A = 0.327 \text{ mm}^2$) and one thin ($A = 0.128 \text{ mm}^2$). Select a length of nichrome wire and place it in your circuit (so that it is connected to the power supply and in series with the ammeter). The effective length of the wire is the distance between the two clips that connect it to the circuit (to vary the length of the wire, simply move the clips closer together).
2. Write the loop rule equation for this circuit and use it to predict the current that will be driven by a voltage of 1 V. Your prediction should also include an uncertainty, due to the uncertainty in your length measurements and the uncertainty in your r_{wires} measurement. The uncertainty is given by:

$$\Delta i = \frac{\varepsilon}{i} \sqrt{\left(\frac{\Delta L}{nAu}\right)^2 + \Delta r_{\text{wires}}^2}$$

$$\frac{L}{nAu} + r_{\text{wires}}$$

This calculation is done for you in the provided spreadsheet.

Wire		Predicted Current		Measured Current	
		Mean	Uncert.	Mean	Uncert.
Long Thick	+	-	-	-	-
Short Thick	+	-	-	-	-
Long Thin	+	-	-	-	-
Short Thin	+	-	-	-	-

Table 2

3. Turn on the power supply and measure the current. Record your value. Remember to record both mean and uncertainty.
4. Repeat your prediction and measurement three more times, varying the length and thickness of the wire until you have filled out Table 2.

Analysis

1. Were your predictions consistent with your measurements? Why or why not? Be quantitative.
2. How fast were the electrons moving, on average, through the long, thick wire? What was the electric field in the wire?