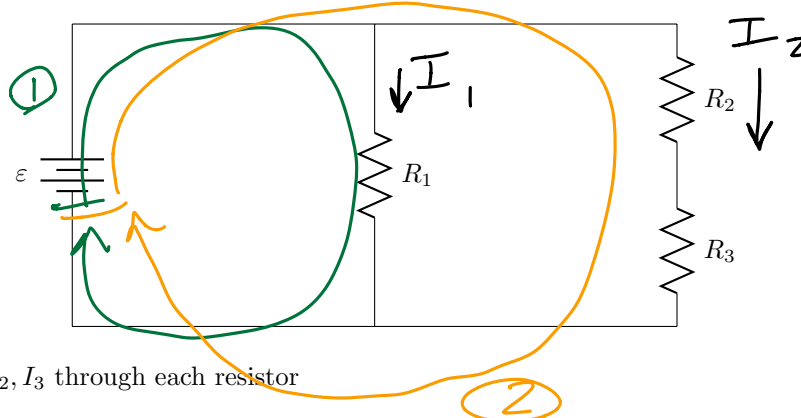


Quiz 6

In the following diagram: $R_1 = 10 \Omega$, $R_2 = 10 \Omega$, and $R_3 = 5 \Omega$. The battery emf $\varepsilon = 3.0 \text{ V}$.



1. Find the currents I_1, I_2, I_3 through each resistor
2. Find the potential difference ΔV across each resistor
3. Find the power dissipated through each resistor

$$\begin{aligned} \textcircled{1} \quad & \varepsilon - I_1 R_1 = 0 \\ & I_1 = \frac{\varepsilon}{R_1} = \frac{3}{10} \text{ A} \\ \textcircled{2} \quad & \varepsilon - I_2 R_2 - I_2 R_3 = 0 \\ & I_2 = I_3 = \frac{\varepsilon}{R_2 + R_3} = \frac{3}{15} = \frac{1}{5} \text{ A} \end{aligned}$$

$$\textcircled{2} \quad \Delta V_1 = I_1 R_1 = \left(\frac{3}{10}\right)(10) = 3 \text{ V}$$

$$\Delta V_2 = I_2 R_2 = \left(\frac{1}{5}\right)(10) = 2 \text{ V}$$

$$\Delta V_3 = I_2 R_3 = \left(\frac{1}{5}\right)(5) = 1 \text{ V}$$

$$\textcircled{3} \quad P = IV = I^2 R$$

$$P_1 = I_1 V_1 = \frac{3}{10} (3) = \boxed{\frac{9}{10} \text{ W}}$$

also:

$$P_1 = I_1^2 R_1 = \left(\frac{3}{10}\right)^2 10 = \boxed{\frac{9}{10} \text{ W}} \quad \checkmark$$

$$P_2 = I_2 \Delta V_2 = \left(\frac{1}{5}\right) (2) = \boxed{\frac{2}{5} \text{ W}}$$

$$= I_2^2 R_2 = \left(\frac{1}{5}\right)^2 (10) = \frac{10}{25} = \boxed{\frac{2}{5} \text{ W}} \quad \checkmark$$

$$P_3 = I_2 \Delta V_3 = \frac{1}{5} (1) = \boxed{\frac{1}{5} \text{ W}}$$

$$= I_2^2 R_3 = \left(\frac{1}{5}\right)^2 (5) = \boxed{\frac{1}{5} \text{ W}}$$